
## General PIR Application Schematics

The following circuits are very simple and basic PIR applications without bells and whistles.

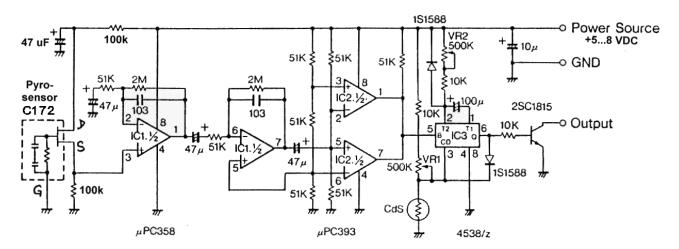
## 1 Standard PIR circuit configuration

A typical motion detector circuit with two-stage amplifier, window comparator and output timer. This configuration could be used for human body sensoring which is used by light switches.


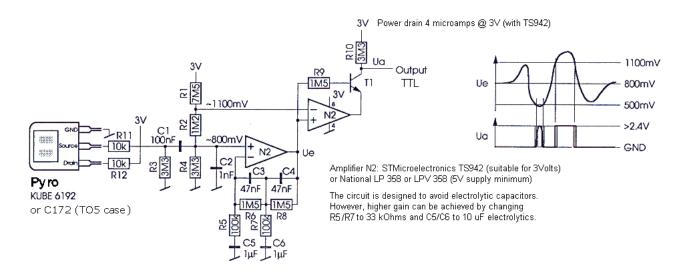
## 2 Low power/voltage circuit


This low power/voltage circuit can be used for low and medium range applications.



Feb 09 1/2
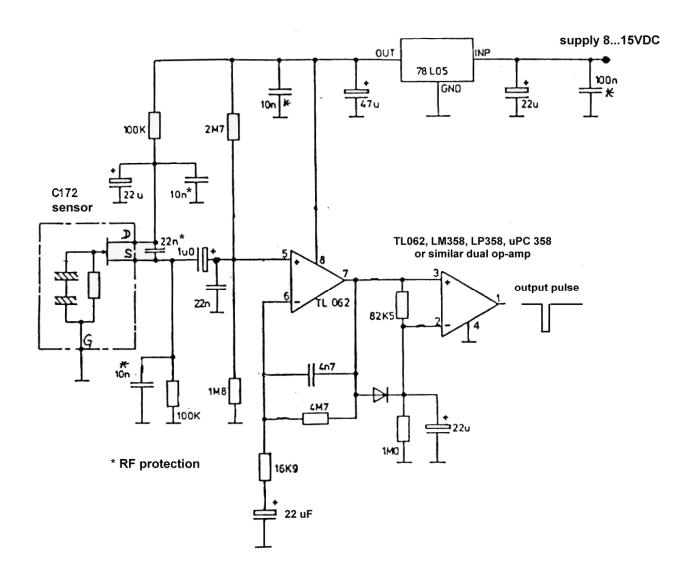
## 3 Simplified PIR circuit

This simplified PIR circuit delivers an output pulse when motion is detected.



Feb 09 2/2